 


# Mixed Analog-Digital VLSI Mini-project 1: 2-Input AND Gate


Qingmu Deng

February 11, 2021

## 1 Schematic Capture and Simulation




(a) Inverter symbol created in Xschem.

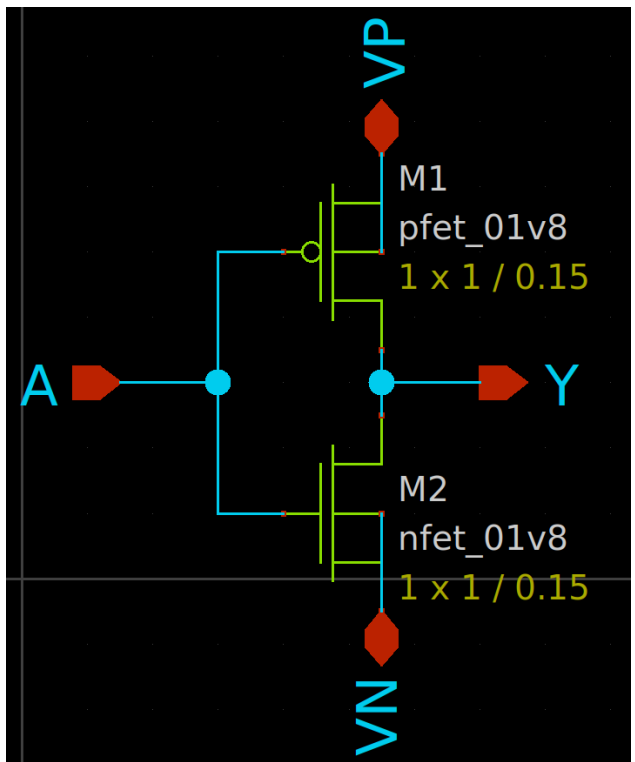


(b) Inverter schematic created in Xschem.

Figure 1: Inverter design in Xschem.

 To begin with, I implemented an inverter design shown in Figure 1 as introduced by Professor Minch in his tutorial video. Similarly, I independently created a hierarchy schematic for NAND2 as shown in Figure 2.



(a) NAND2 symbol created in Xschem.

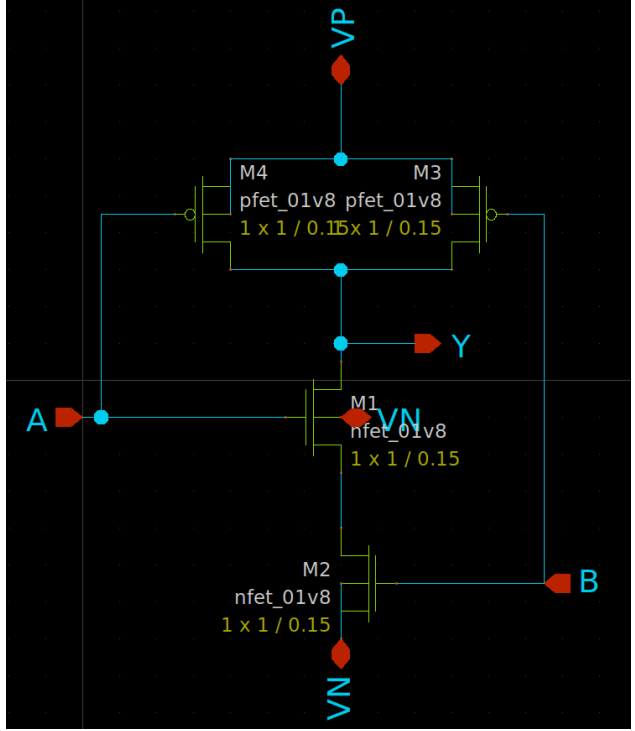

(b) NAND2 schematic created in Xschem.

Figure 2: NAND2 design in Xschem.

I created an AND2 gate by inverting the output of NAND2 with the inverter. You can see the test harness of the AND2 gate in Figure 3.  $V_{DD}$  is set to be 1.8 V, and the square waves at NAND2 inputs switches between 0 V and 1.8 V. To capture all four possible inputs, {00, 01, 10, 11}, to be presented to this two-input gate, the square wave at the input node  $V_B$  is set to have twice the period of  $V_A$ . The output node  $V_{out}$  is loaded with a 200 fF capacitor as specified.

As you can see for the simulation results in Figure 4, the only time where  $V_{out}$  outputs high is when both  $V_A$  and  $V_B$  outputs high. This follows out expectation of how an AND2 gate should behave.

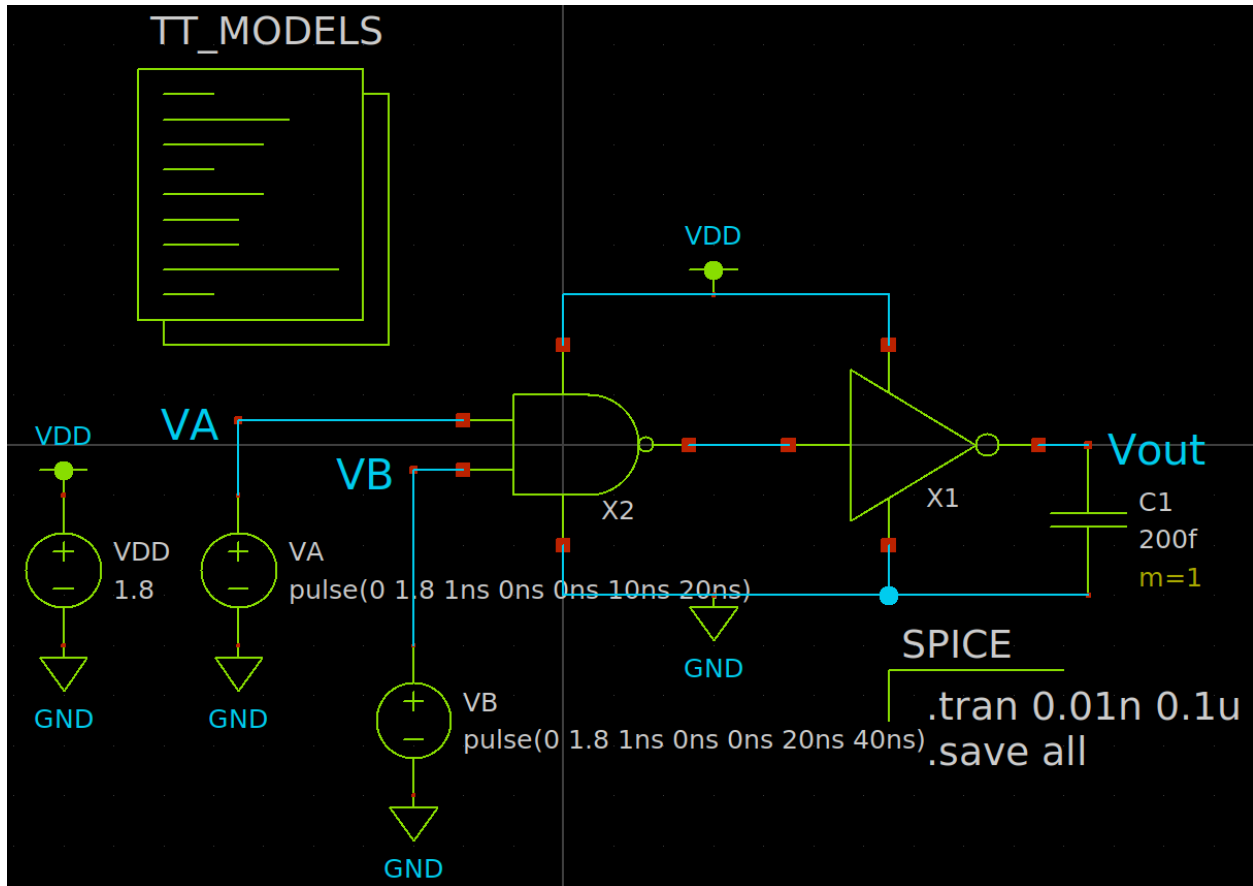


Figure 3: The simulation setup of a AND2 gate made of a NAND2 and an inverter.

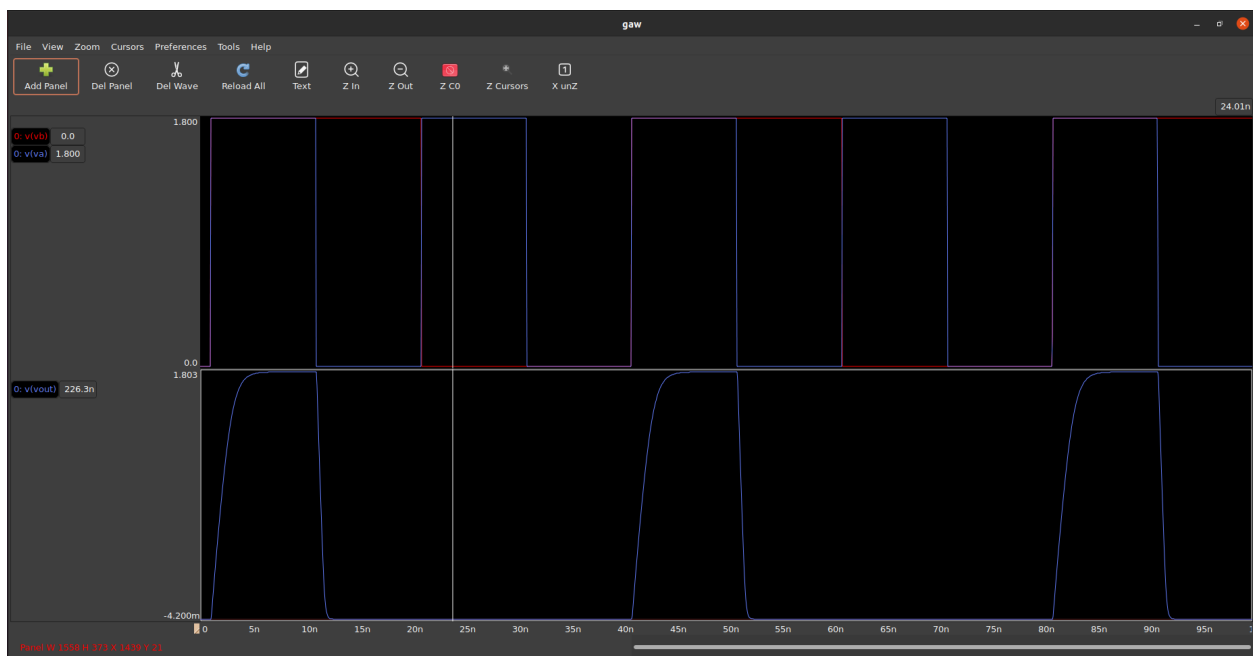


Figure 4: The simulation AND2 gate behavior view in *gaw*.

## 2 Layout Design

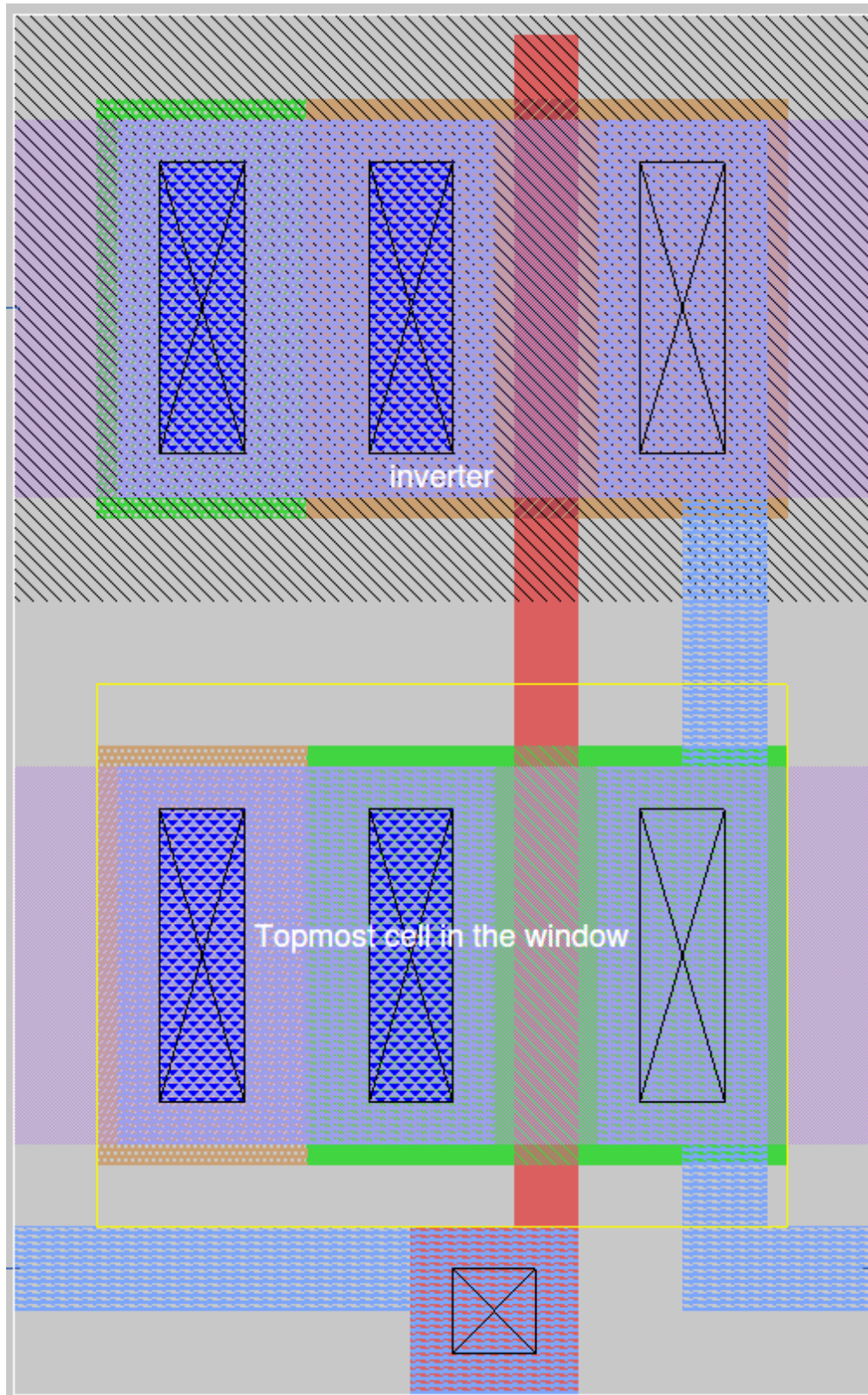


Figure 5: *Magic* layout of the inverter.

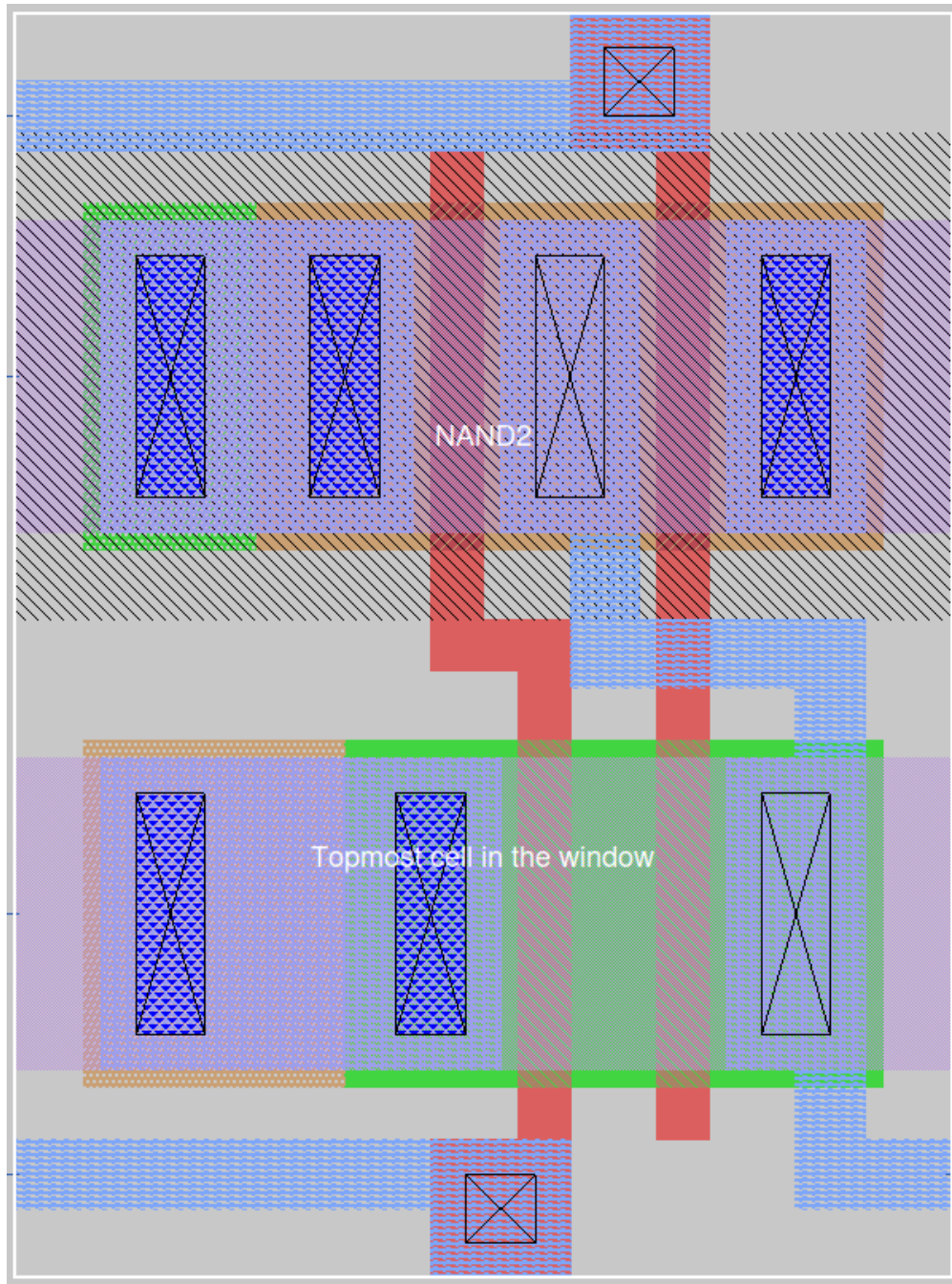


Figure 6: *Magic* layout of the NAND2.



 


Figure 7: *Magic* layout of the AND2 by combining NAND2 and inverter layouts.

### 3 Layout versus Schematic